

Experiment No. 4


Adders and Subtractors

Hardware runs

Run 1: Half adder (30 mins)

A half adder is a circuit capable of adding two 1-bit numbers to produce a 1-bit sum and a 1-bit carry. Write down the truth table of a half adder and draw its diagram

Diagram

 


Truth Table

| A | B | SUM | CARRY |
|---|---|-----|-------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

Run 2: Half subtractor (20 mins)

Analogous to adders, a half subtractor performs subtraction on 2-bits while a full subtractor operates on 3-bits. Write the truth table of a Half subtractor below and Draw the circuit diagram

Diagram

 

Truth Table

| A | B | DIFFERENCE | BORROW |
|---|---|------------|--------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |

Software runs


Run 3: Full adder and 4-bit adder (20 Mins)


- Write the Verilog code and testbench of Full adder using data flow modeling. (Hint: $\text{Sum} = A \oplus B \oplus C$, $\text{Carry} = C(A \oplus B) + AB$)
- Write the Verilog code and testbench for 4-bit parallel adder using structural modeling, use full adder as a building block defined in above code file.

(This is using or calling module from another file)

Run 4: BCD adder (25 Mins)

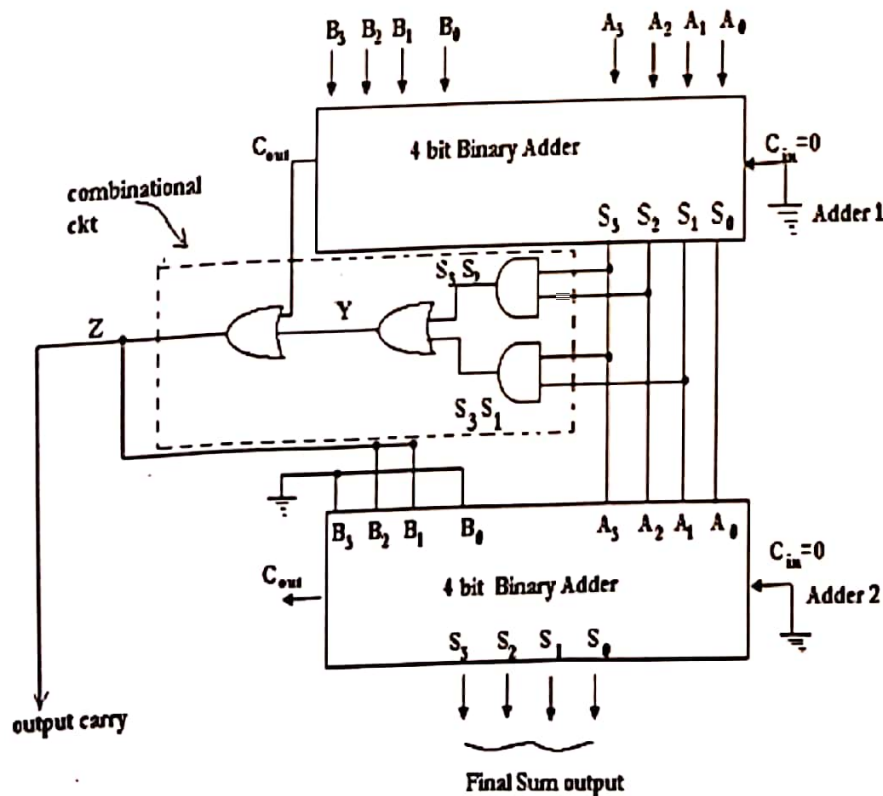- Write the verilog code and testbench for BCD adder using structural modeling, use 4-bit parallel adder and other gates as building blocks. Use parallel adder code from above file)(Hint refer the image below)



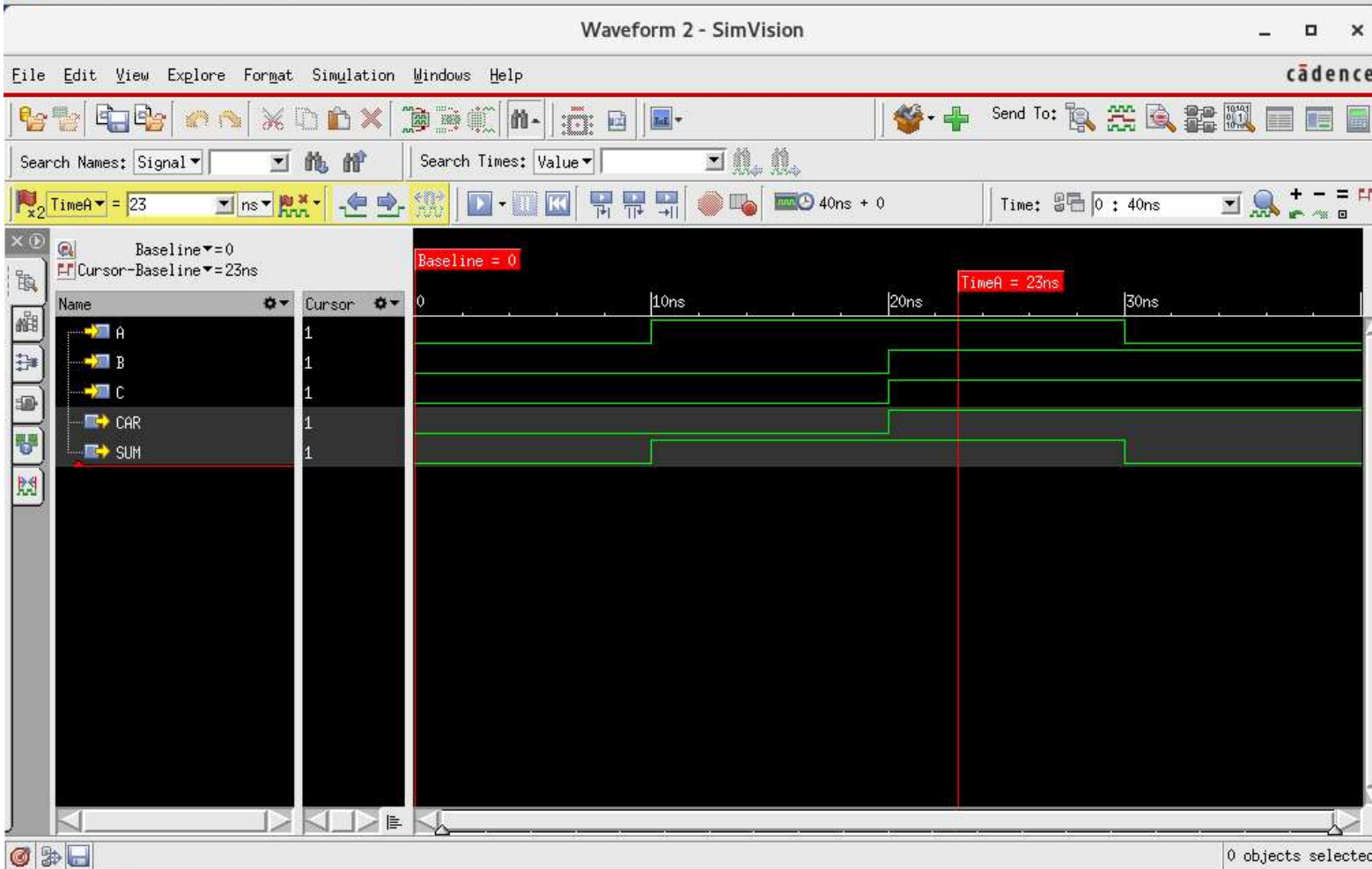

Top Level Design

Library

arsh3

Simulation Mode

☐ Batch☒ Interactive (Choose Steps):

Compile



Elaborate



Simulate

9 Simulate

```
xcelium> probe -create -shm testbench,U1,A testbench,U1,B testbench,U1,C testbench,U1,CAR testbench,U1,SUM
Created probe 2
xcelium> run
Simulation stopped via $stop(1) at time 40 NS + 0
xcelium>
```

SimVision simulator

L26

C24

R:

7
CENTO

Design Browser 1 - SimVision

Waveform 1 - SimVision

File Edit View Explore Format Simulation Windows Help

Search Names: Signal Search Times: Value

TimeA = 23 ns 40ns + 0 Time: 0 : 40ns

Baseline = 0

Cursor-Baseline = 23ns

| Name | Cursor |
|------|--------|
| A0 | 1 |
| A1 | 1 |
| A2 | 1 |
| A3 | 0 |
| B0 | 0 |
| B1 | 1 |
| B2 | 1 |
| B3 | 1 |
| C0 | x |
| C1 | x |
| C2 | x |
| C3 | x |
| C4 | 0 |
| S0 | x |
| S1 | x |
| S2 | x |
| S3 | x |

Simulation stopped via stop() at time 40 ns 0.000 xcelium>

Simulation Mode

Batch

Interactive (Choose Steps):

Compile Elaborate Simulate

3 Generate Netlist

0 objects selected

functional [verilog.v (~/...)] user5@dsp5... Virtuoso® 6... Text Editor (...)

Waveform 1... 1 / 4

user5@dsp5:~/arsh

File Edit View

[user5@dsp5 ~]
[user5@dsp5 a
WARNING fil
WARNING fil
WARNING fil

Text Editor (Verilog) Verilog-Editor Editing: arsh3 lab4_1 functional

Launch File Edit View Create Check Options Window Help

Basic

Navigator

Summary

OBJECTS

GROUPS

Cells

Types

```
//Verilog HDL for "arsh3", "lab4_1" "functional"

module lab4_1 (A0,A1,A2,A3,B0,B1,B2,B3,C0,C4,S0,S1,S2,S3);
  input A1,A2,A3,A0,B0,B1,B2,B3,C0;
  output S0,S1,S2,S3,C4;
  wire C1,C2,C3;

  Add P1(C0,A0,B0,S0,C1);
  Add P2(C1,A1,B1,S1,C2);
  Add P3(C2,A2,B2,S2,C3);
  Add P4(C3,A3,B3,S3,C4);

endmodule

module Add(A,B,C,SUM,CAR);
  input A,B,C;
  output CAR,SUM;
  assign SUM= A^B^C;
  assign CAR=(C&(A^B))+A&B;
endmodule

//testbench
module testbench;
  reg A0,A1,A2,A3,B0,B1,B2,B3,C0;
  wire S0,S1,S2,S3,C4;
  initial
  begin
    A0=0;A1=0;A2=0;A3=0;B0=0;B1=0;B2=0;B3=0;C0=0;
    #10 A0=1;A1=0;A2=0;A3=0;B0=1;B1=0;B2=1;B3=1;
    #10 A0=1;A1=1;A2=1;A3=0;B0=0;B1=1;B2=1;B3=1;
    #10 A0=1;A1=1;A2=1;A3=1;B0=1;B1=0;B2=0;B3=1;
    #10 $stop;
  end
  lab4_1 U1( A0,A1,A2,A3,B0,B1,B2,B3,C4,S0,S1,S2,S3);
endmodule
```

mouse L: 1(2) > M: R: L1 C1



Home



surya



Trash



samay



arsh

Text Editor (Verilog) Verilog-Editor Editing: arsh3 lab4 functional *

Launch File Edit View Create Check Options Window Help

Basic

Navigator

Summary

OBJECTS

GROUPS

Cells

Types

```
//Verilog HDL for "arsh3", "lab4" "functional"

module lab4 (SUM,CAR,A,B,C);
  input A,B,C;
  output SUM,CAR;
  assign SUM=A^B^C;
  assign CAR= C&(A^B)|(A&B);
endmodule

//testbench

module testbench;
  reg A,B,C;
  wire SUM,CAR;
  initial
  begin
    A=0;
    B=0;
    C=0;
    #10 A=1;B=0;C=0;
    #10 A=1;B=1;C=1;
    #10 A=0;B=1;C=1;
    #10 $stop;
  end
  lab4 U1(A,B,C,SUM,CAR);
endmodule
```

mouse L: M: R:

1(2) > L28 C1

7
CENTO

1. <https://www.edaplayground.com/x/BMaW>
2. <https://www.edaplayground.com/x/axR9>
3. https://www.edaplayground.com/x/gMD_